
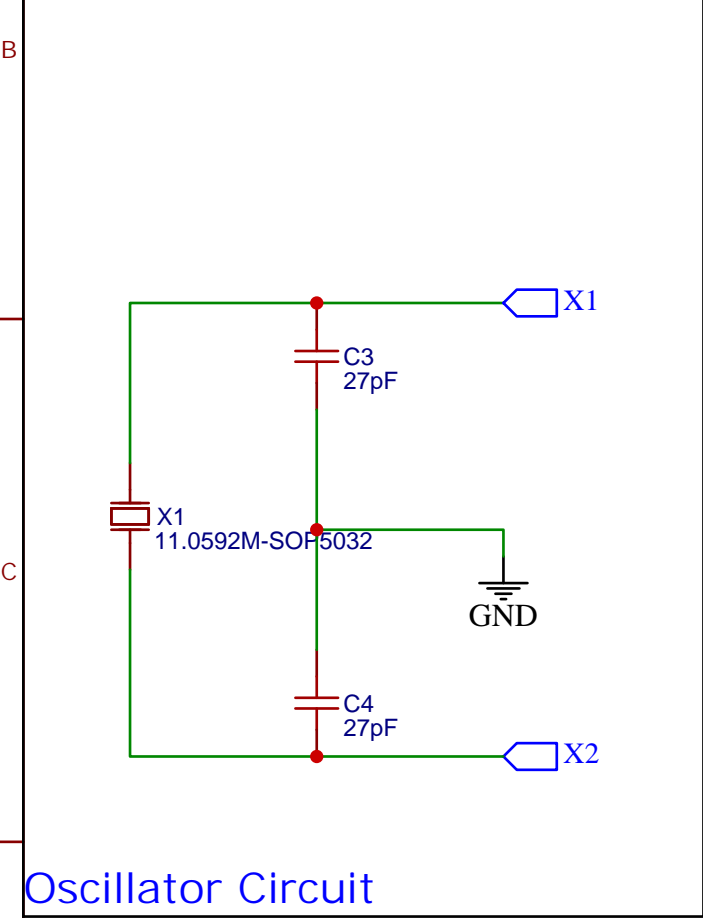


Power Supply Circuit

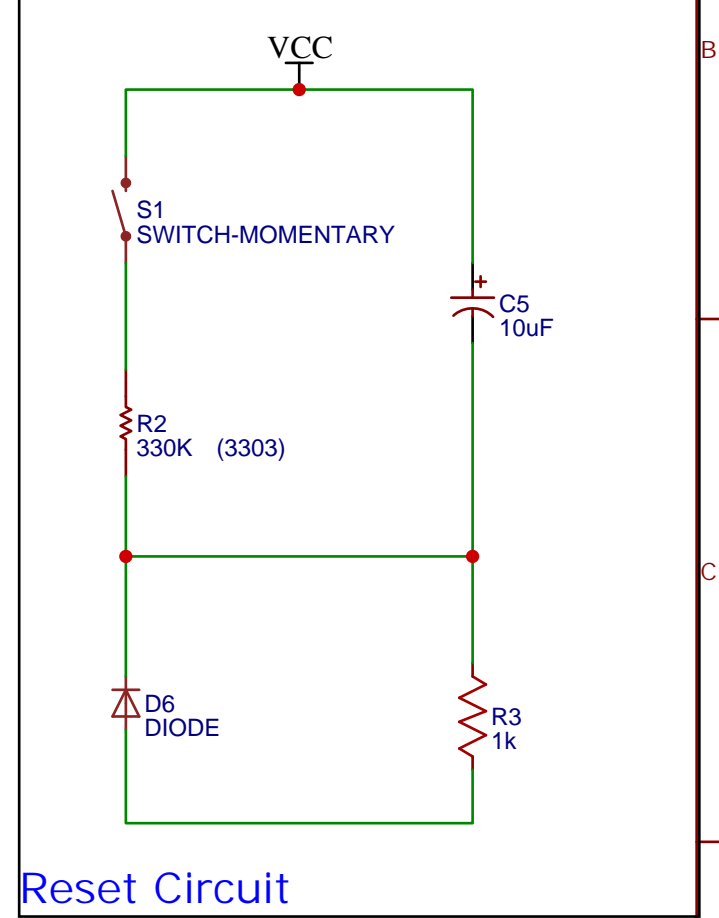


Oscillator Circuit




Reset Circuit

TITLE: Lab1_Part3_Schematic_1		REV: 1.0
	Company: University of Colorado Boulder	Sheet: 1/2
	Date: 2022-02-06	Drawn By: Abijith A

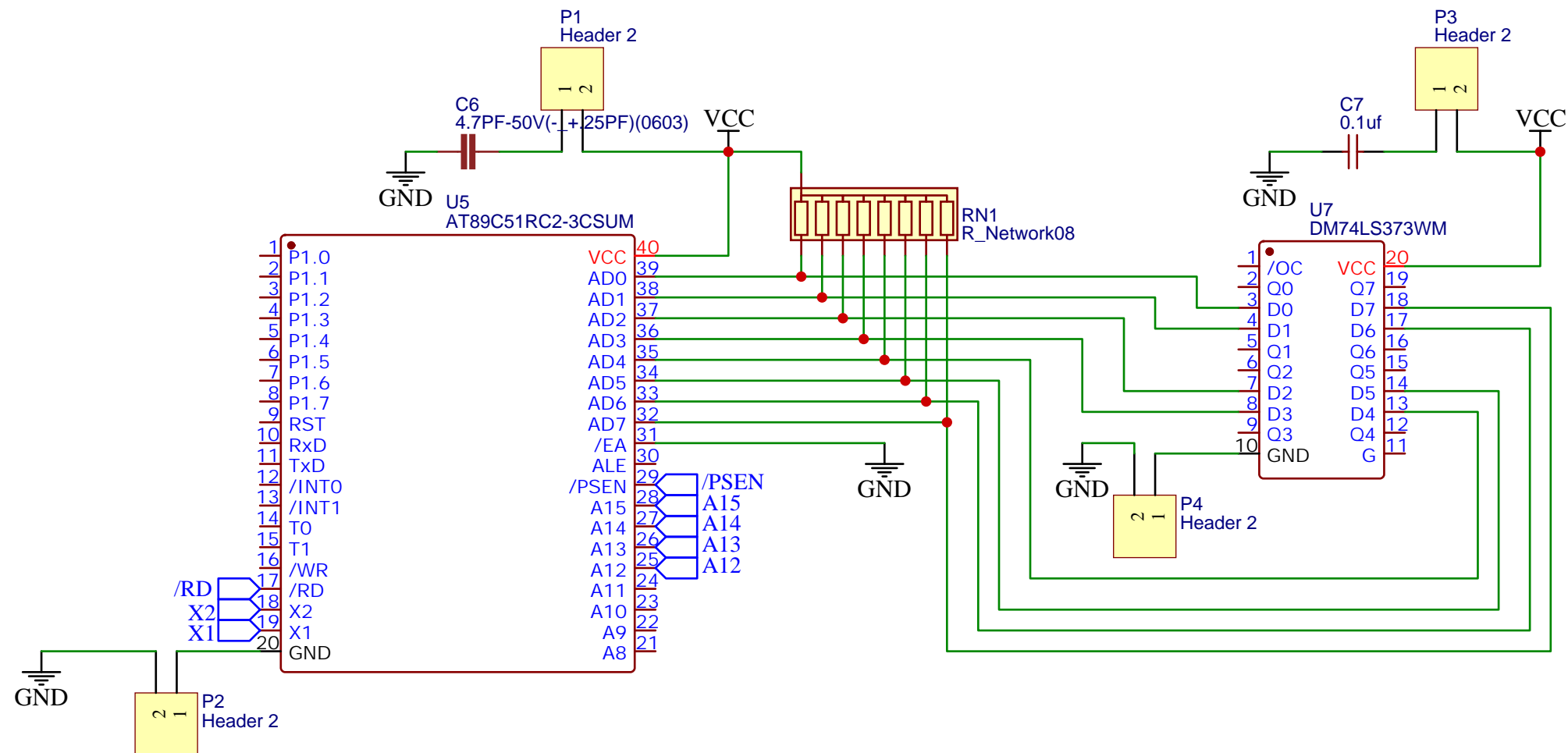

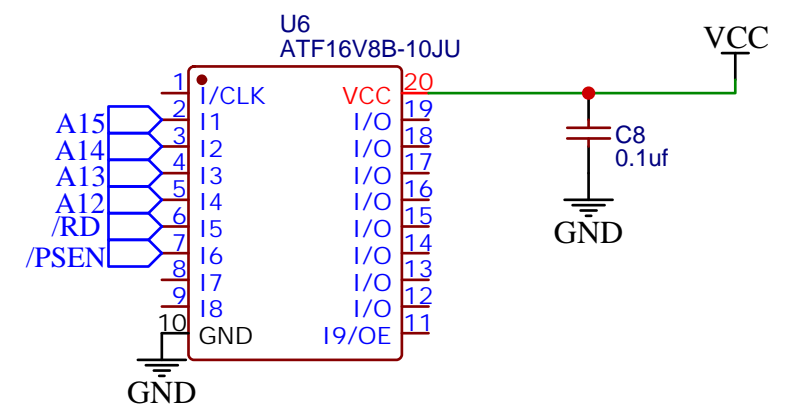Microchip (Atmel) AT89C51RC2, DIP-40 and 74LS373, Transparent Latch, Tri-state, DIP-20



Microchip (Atmel) ATF16V8C SPLD, DIP-20

TITLE: Lab1_Part3_Schematic_2		REV: 1.0
EasyEDA	Company: University of Colorado Boulder	Sheet: 2/2
	Date: 2022-02-06	Drawn By: Abijith A